We use KVL from the output node down to ground to find an expression for $v_{\rm gs2}$.

$$v_{\rm gs2} = v_{\rm out} + v_{\rm gs1} \tag{37}$$

KCL at the tail node:

$$g_{\rm m1}v_{\rm gs1} + g_{\rm m2}v_{\rm gs2} + g_{\rm ds2}v_{\rm gs2} + g_{\rm ds5}v_{\rm gs2} = 0$$
(38)

Using Equation 37 to substitute $v_{\rm gs2}$ in {#eq-app-vbufzout-kcl-vtail-cl} we find an equation for $v_{\rm gs1}$.

$$v_{\rm gs1} = -\frac{g_{\rm m2} + g_{\rm ds2}}{g_{\rm m1} + g_{\rm m2} + g_{\rm ds2} + g_{\rm ds5}} v_{\rm out}$$
(39)

Again, we derive the output conductance by plugging Equation 37, Equation 30 and Equation 39 step by step into Equation 36. First, we use Equation 37 to eliminate $v_{\rm gs2}$.

$$i_{\rm out} - \left(g_{\rm ds4} + g_{\rm ds2} + g_{\rm m2}\right)v_{\rm out} - g_{\rm m34}v_{\rm gs34} - \left(g_{\rm ds2} + g_{\rm m2}\right)v_{\rm gs1} = 0$$

Second, Equation 30 also holds for the closed-loop case and lets us eliminate v_{gs34} .

$$i_{\text{out}} - (g_{\text{ds4}} + g_{\text{ds2}} + g_{\text{m2}}) v_{\text{out}} - (g_{\text{ds2}} + g_{\text{m2}} - g_{\text{m1}}) v_{\text{gs1}} = 0$$

Third, we use Equation 39 to eliminate the remaining unknown v_{gs1} .

$$i_{\rm out} - \left(g_{\rm ds4} + g_{\rm ds2} + g_{\rm m2}\right)v_{\rm out} + \left(g_{\rm ds2} + g_{\rm m2} - g_{\rm m1}\right)\frac{g_{\rm m2} + g_{\rm ds2}}{g_{\rm m1} + g_{\rm m2} + g_{\rm ds2} + g_{\rm ds5}}v_{\rm out} = 0$$

A more simpler result can be obtained, if we neglect $g_{\rm ds2}$ and $g_{\rm ds5}$ in Equation 39 first $(g_{\rm m}\gg g_{\rm ds})$ and then plug it into our main equation. Additionally, we use $g_{\rm m12}=g_{\rm m1}=g_{\rm m2}$ to further simplify the equation.

$$i_{\rm out} - \left(g_{\rm ds4} + \frac{3}{2}g_{\rm ds2} + g_{\rm m12}\right)v_{\rm out} \approx 0$$

If we apply $g_{\rm m}\gg g_{\rm ds}$ again, we arrive at the same result which was used for the noise calculation in Section 7.3, compare the expression for $Y'_{\rm load}$ given by Equation 20 .

$$i_{\text{out}} - (g_{\text{m12}}) v_{\text{out}} \approx 0$$

17 Appendix: ngspice Cheatsheet

Here is an unsorted list of useful ngspice settings and command:

17.1 Commands

- ac dec|lin points fstart fstop performs a small-signal ac analysis with either linear or decade sweep
- dc sourcename vstart vstop vincr [src2 start2 stop2 incr2] runs a dc-sweep, optionally across two variables
- display shows the available data vectors in the current plot
- echo can be used to display text, \$variable or \$&vector, can be useful for debugging
- let name = expr to create a new vector; unlet vector deletes a specified vector; access vector data with \$&vec
- linearize vec linearizes a vector on an equidistant time scale, do this before an FFT; with set specwindow=windowtype a proper windowing function can be set
- meas can be used for various evaluations of measurement results (see ngspice manual for details)
- noise v(output <ref>) src (dec|lin) pts fstart fstop runs a small-signal noise analysis
- op calculates the operating point, useful for checking bias points and device parameters
- plot expr vs scale to plot something
- print expr to print it, use print all to print everything
- remzerovec can be useful to remove vectors with zero length, which otherwise cause issues when saving or plotting data
- rusage plot information about resource usage like memory
- save all or save signal specifies which data is saved during simulation; this lowers RAM usage during simulation and size of RAW file; do save before the actual simulation statement
- setplot show a list of available plots
- set var = value to set the value of a variable; use variable with \$var; unset var removes a variable
- set enable_noisy_r to enable noise of behavioral resistors; usually, this is a good idea
- shell cmd to run a shell command
- show : param, like show : gm shows the $g_{\rm m}$ of all devices after running an operating point with op
- spec plots a spectrum (i.e. frequency domain plot)
- status shows the saved parameters and nodes
- tf runs a transfer function analysis, returning transfer function, input and output resistance
- tran tstep tstop <tstart <tmax>> runs a transient analysis until tstop, reporting results with tstep step size, starting to plot at tstart and performs time steps not larger then tmax
- wrdata writes data into a file in a tabular ASCII format; easy to further process
- write writes simulation data (the saved nodes) into a RAW file; default is binary, can be changed to ASCII with set filetype=ascii; with set appendwrite data is added to an existing file

17.2 Options

Use option option=val option=val to set various options; important ones are:

- abstol sets the absolute current error tolerance (default is 1pA)
- gmin is the conductance applied at every node for convergence improvement (default is 1e-12); this can be critical for very high impedance circuits
- klu sets the KLU matrix solver
- list print the summary listing of the input data
- maxord sets the numerical order of the integration method (default is 2 for Gear)
- method set the numerical integration method to gear or trap (default is trap)
- node prints the node table
- opts prints the option values
- temp sets the simulation temperature
- reltol set the relative error tolerance (default is 0.001 = 0.1%)
- savecurrents saves the terminal currents of all devices
- sparse sets the sparse matrix solver, which can run noise analysis, but is slower than
- vntol sets the absolute voltage error tolerance (default is $1\mu V$)
- warn enables the printing of the SOA warning messages

17.3 Convergence Helper

- option gmin can be used to increase the conductance applied at every node
- option method=gear can lead to improved convergence
- .nodeset can be used to specify initial node voltage guesses
- .ic can be used to set initial conditions

18 Appendix: Xschem Cheatsheet

When opening Xschem, using Help -> Keys a pop-up windows comes up with many useful shortcuts. The most useful are:

18.0.0.1 Moving around in a schematic:

- Cursor keys to move around
- Ctrl-e to go back to parent schematic
- e to descend into selected symbol
- f full zoom on schematic
- Shift-z to zoom in
- Ctrl-z to zoom out